


EELE 250: Circuits, Devices, and Motors

Op Amps (cont.)

Assignment Reminder


- Read 14.7 and 14.9; also read 5.7 (3 phase)
- Practice Problems:
 - P14.74, P14.75
- Lab #7 this week. A formal lab report for Lab #7 is due at your lab time Nov. 14-18.
- Exam #3: Wednesday, November 9, in class. The coverage will be amplifier concepts and operational amplifier circuit analysis.

Clicker quiz

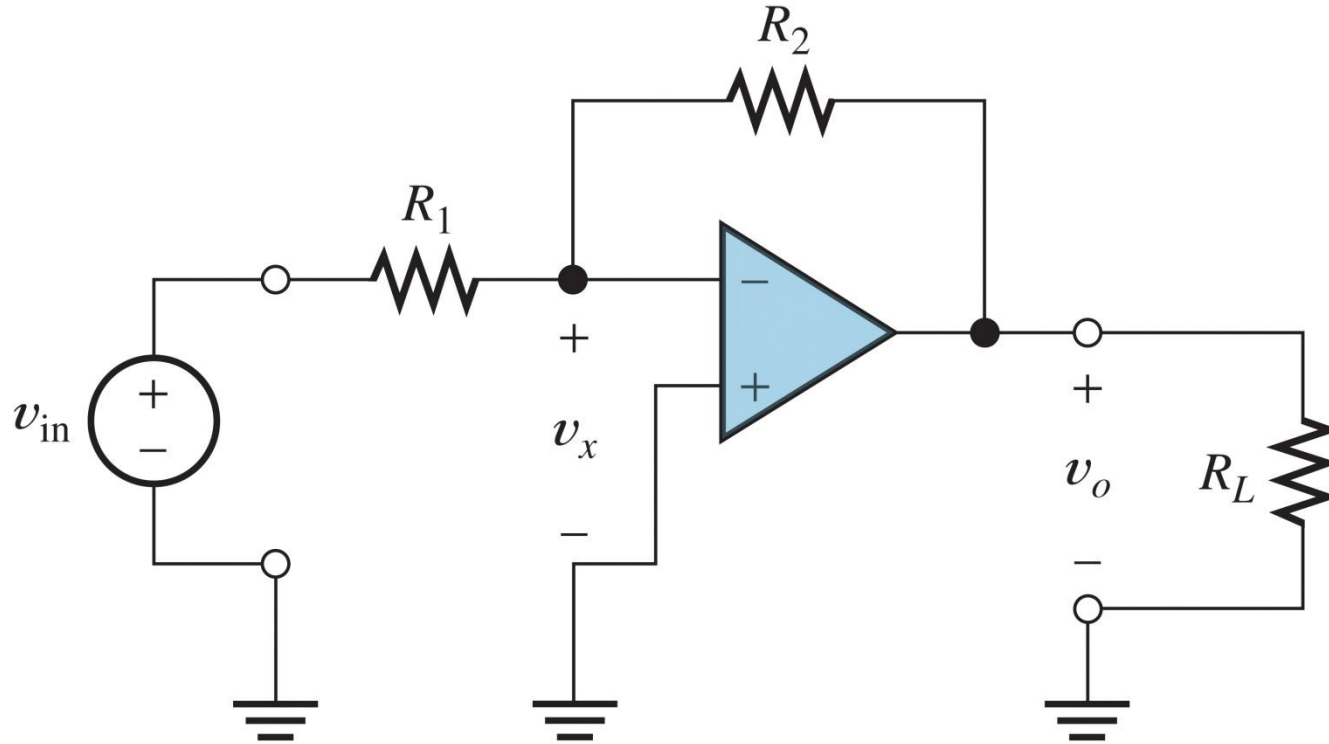


- (a) $V_o = -R_L V_{in}$
- (b) $V_o = -V_{in}$
- (c) $V_o = -(R_2/R_1) V_{in}$
- (d) $V_o = -(R_1/R_2) V_{in}$
- (e) $V_o = (1+R_2/R_1) V_{in}$

Clicker quiz

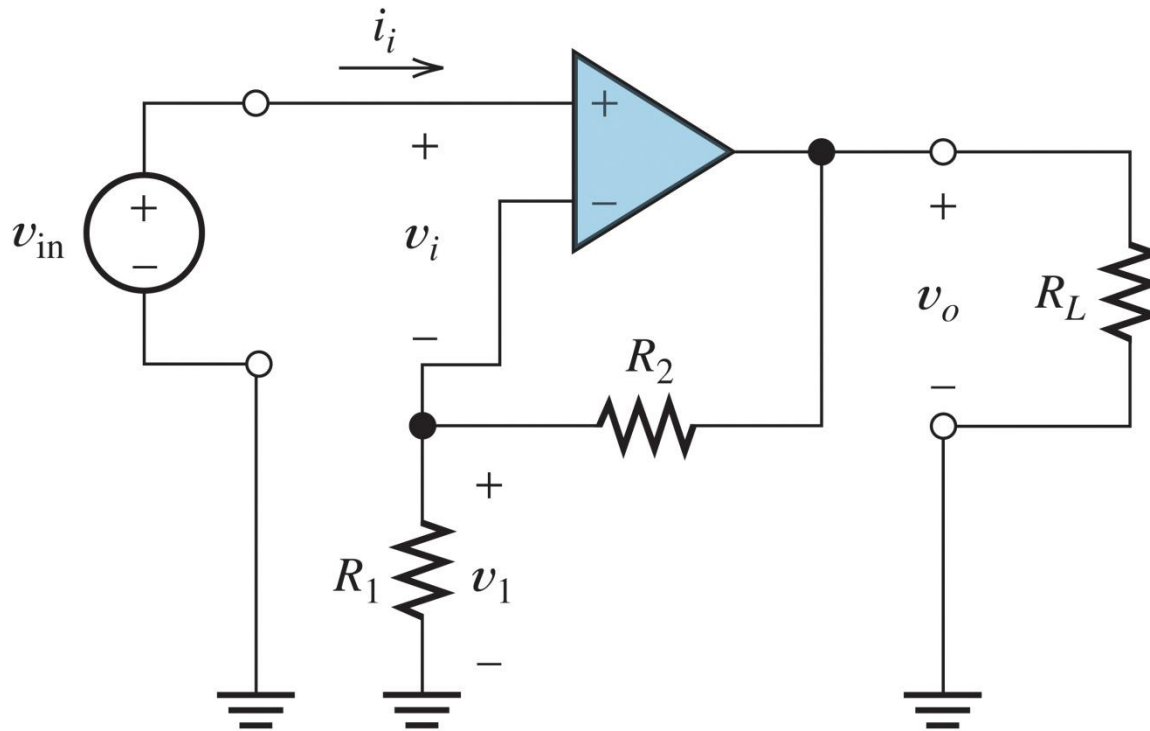

- (a) $V_o = -R_L V_{in}$
- (b) $V_o = -V_{in}$
- (c) $V_o = -(R_2/R_1) V_{in}$
- (d) $V_o = -(R_1/R_2) V_{in}$
- (e) $V_o = (1+R_2/R_1) V_{in}$


Clicker quiz

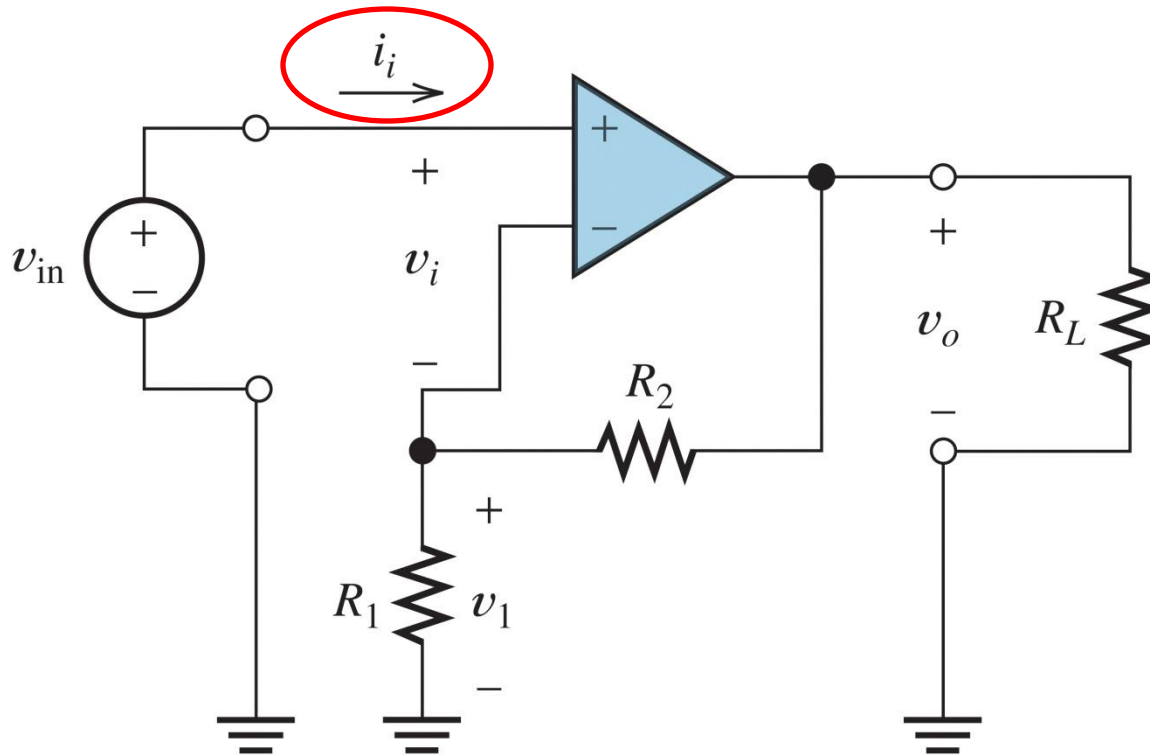

Assuming the ideal op amp model, what is i_i ?

- (a) $i_i = v_o/R_L$
- (b) $i_i = v_1/R_1$
- (c) $i_i = v_{in}/R_1$
- (d) $i_i = 0$


Clicker quiz

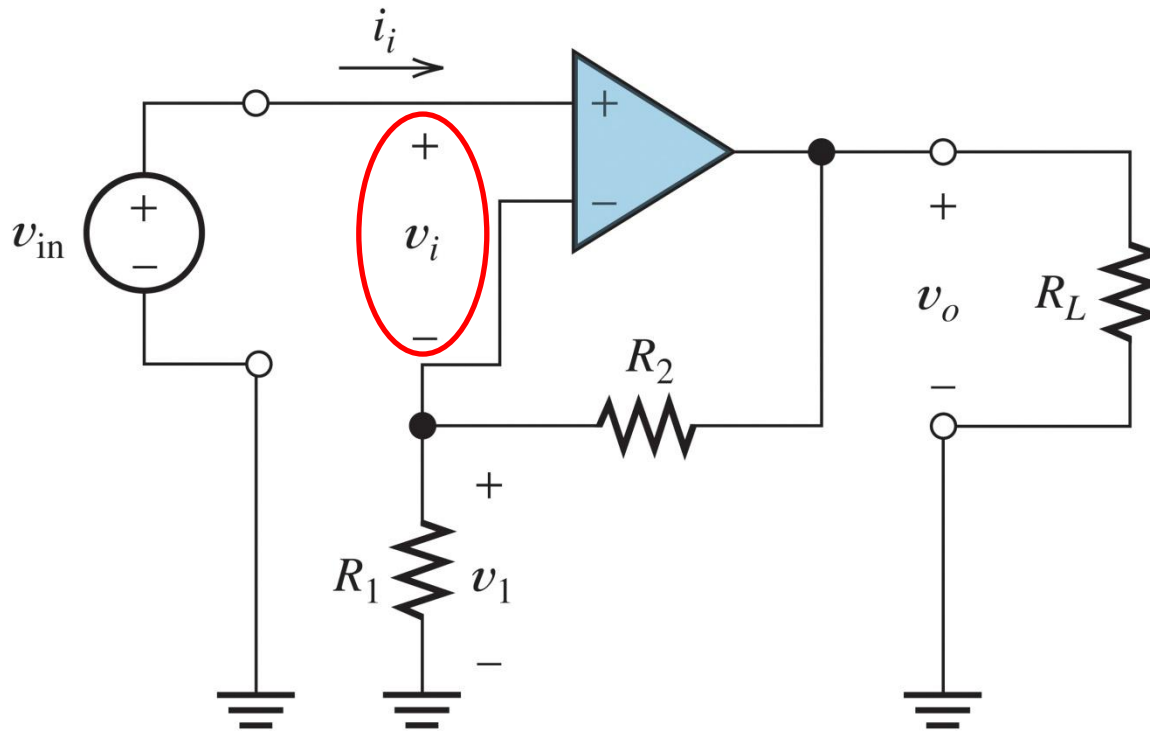

Assuming the ideal op amp model, what is v_i ?

- (a) $v_i = 0$
- (b) $v_i = v_{in}$
- (c) $v_i = -v_{in}$
- (d) $v_i = v_o$

Clicker quiz

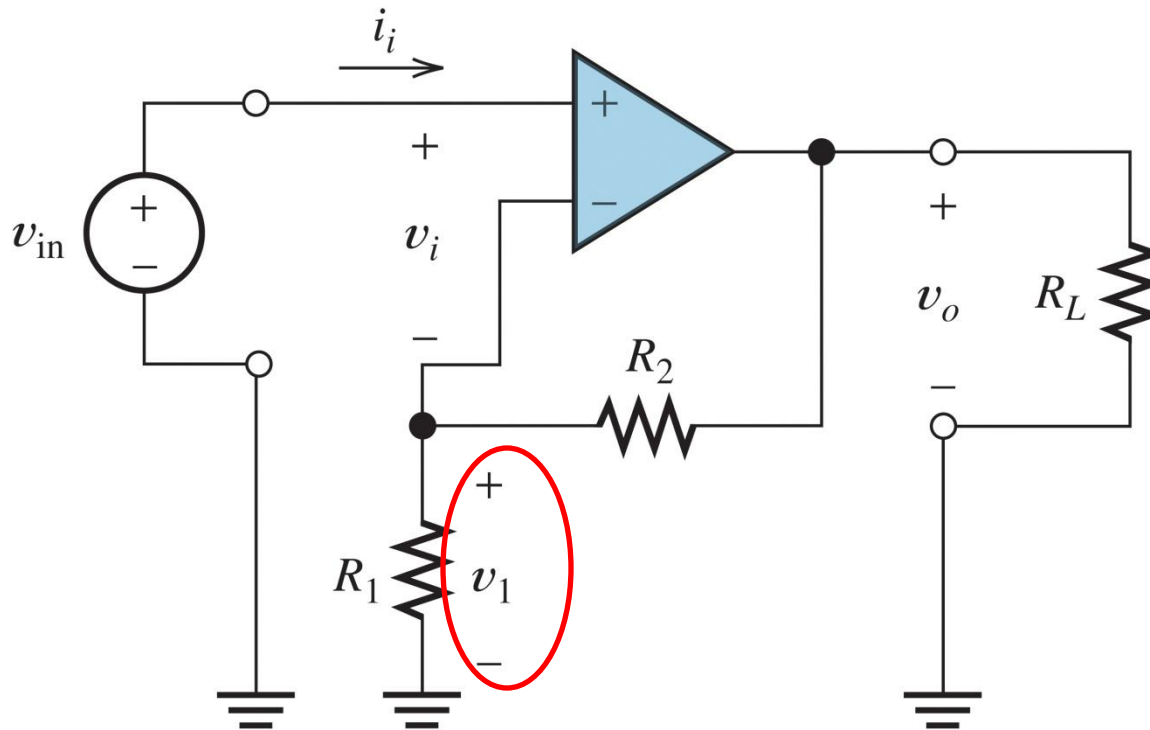

Assuming the ideal op amp model, what is v_1 ?

- (a) $v_1 = v_{in} (R_1 / (R_1 + R_2))$
- (b) $v_1 = v_{in}$
- (c) $v_1 = -v_{in}$
- (d) $v_1 = v_o$



Design with Op Amps

- Typical op amp circuit design involves selecting external resistors to achieve a particular voltage gain, current gain, etc.
- Design involves selecting the best solution from several possible choices. This usually entails tradeoffs and compromises.
- Often choose basic circuits as building blocks:
 - Inverting and non-inverting configuration
 - Voltage follower
 - Summer

Design Example

- We would like to create a control voltage to steer a solar array to point at the sun.
- Two optical sensors: sensors produce a current proportional to how strongly they are illuminated.
 - If the left sensor is illuminated more than the right, we need a proportional POSITIVE voltage.
 - If the right sensor is illuminated more than the left, we need a proportional NEGATIVE voltage.

Design Example (cont.)

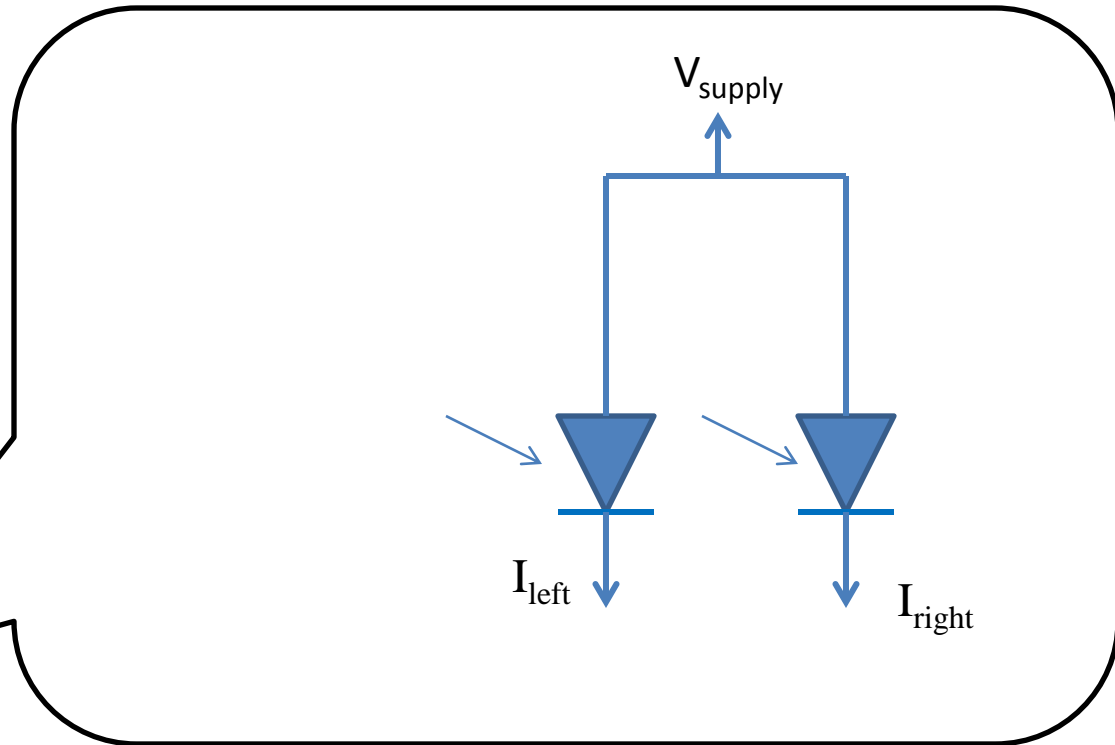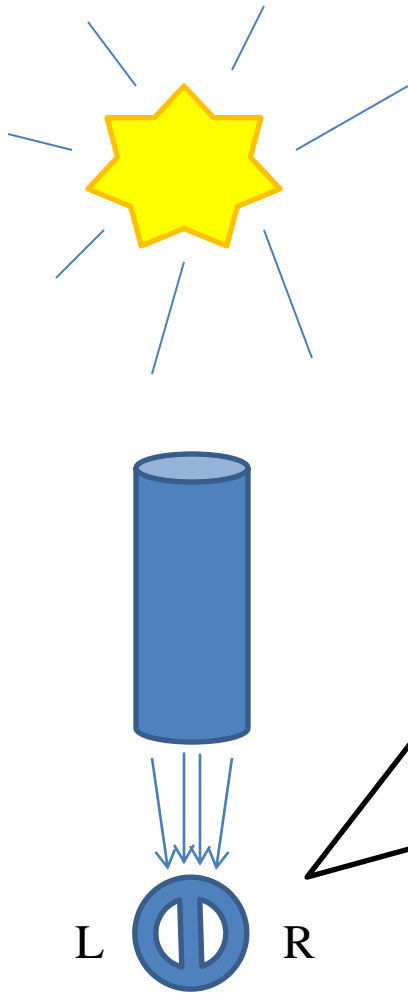

Design Example (cont.)

- Interpretation: We want a circuit that will create a voltage proportional to $(I_{\text{left}} - I_{\text{right}})$
- One idea: convert the currents into voltages, subtract them, and then amplify the result
- Current to voltage converter?
- Summer?

