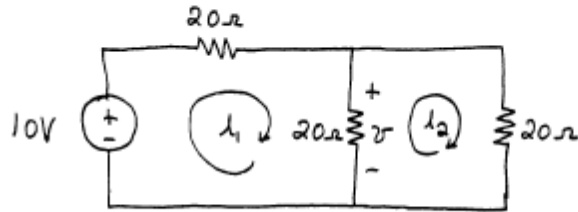


P2.69 Writing and simplifying the mesh equations, we obtain:

$$40i_1 - 20i_2 = 10 \quad -20i_1 + 40i_2 = 0$$



Solving, we find  $i_1 = 0.3333$  and  $i_2 = 0.1667$ .

Thus,  $v = 20(i_1 - i_2) = 3.333 \text{ V}$ .

P2.72 Writing and simplifying the mesh equations yields:


$$14i_1 - 8i_2 = 10$$

$$-8i_1 + 16i_2 = 0$$

Solving, we find  $i_1 = 1.000$  and  $i_2 = 0.500$ .

Finally, the power delivered by the source is  $P = 10i_1 = 10 \text{ W}$ .

P2.77

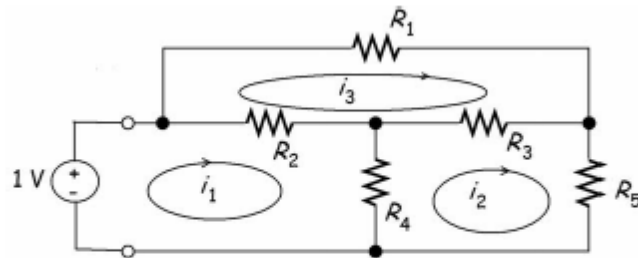

$$\begin{aligned}(R_2 + R_4)i_1 - R_4i_2 - R_2i_3 &= 1 \\ -R_4i_1 + (R_3 + R_4 + R_5)i_2 - R_3i_3 &= 0\end{aligned}$$

$$-R_2i_1 - R_3i_2 + (R_1 + R_2 + R_3)i_3 = 0$$

Now using MATLAB:

R1 = 6; R2 = 5; R3 = 4; R4 = 8; R5 = 2;

R = [(R2+R4) -R4 -R2; -R4 (R3+R4+R5) -R3; -R2 -R3 (R1+R2+R3)];

V = [1; 0; 0];


I = R\V;

Req = 1/I(1) % Gives answer in ohms.

Req =

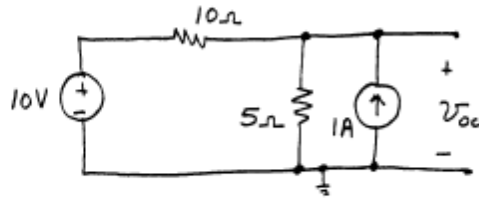4.5979


P2.80\* First, we write a node voltage equation to solve for the open-circuit voltage:




$$\frac{v_{oc} - 10}{10} + \frac{v_{oc}}{5} = 1$$

Solving, we find  $v_{oc} = 6.667 \text{ V}$ .

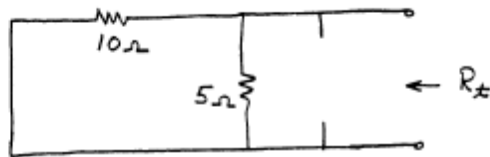
Then zeroing the sources, we have this circuit:



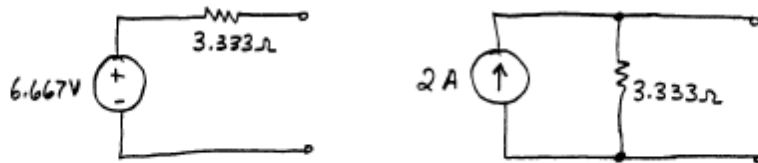Thus,  $R_t = \frac{1}{1/10 + 1/5} = 3.333 \Omega$ . The Thévenin and Norton equivalents are:



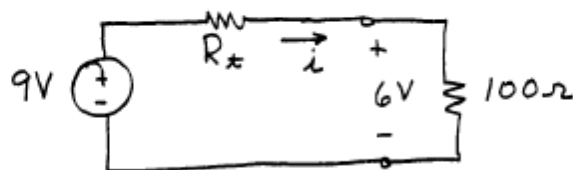P2.81\* The equivalent circuit of the battery with the resistance connected is



$$i = 6/100 = 0.06 \text{ A}$$

$$R_t = \frac{9 - 6}{0.06} = 50 \Omega$$


**P2.83** First, we solve the network with a short circuit:

$$R_{eq} = 10 + \frac{1}{1/10 + 1/15} = 16 \Omega$$


$$i_{10} = 32/R_{eq} = 2 \text{ A}$$

$$i_{15} = i_{10} \frac{10}{10 + 15} = 0.8 \text{ A}$$

$$i_{sc} = i_{15} = 0.8 \text{ A}$$

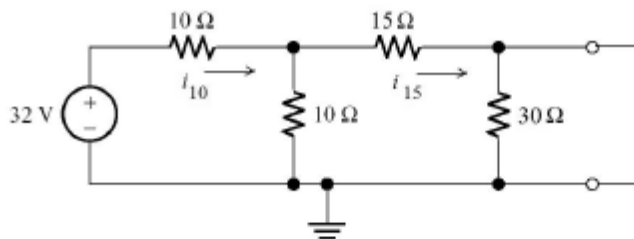


Zeroing the source, we have:

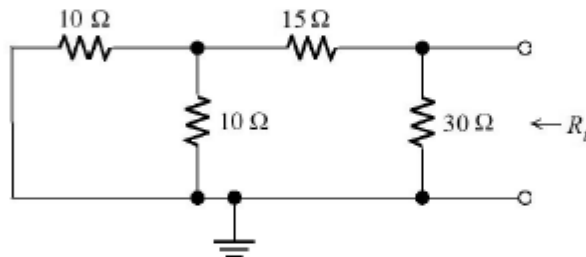


Combining resistances in series and parallel we find  $R_t = 12 \Omega$ .

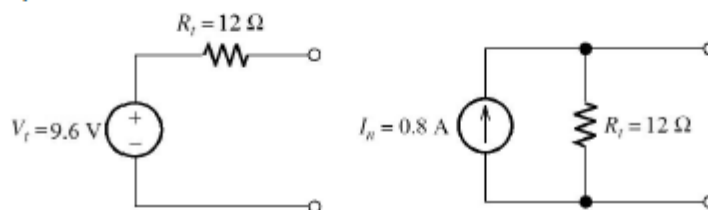Then the Thévenin voltage is  $v_t = i_{sc} R_t = 9.6 \text{ V}$ . The Thévenin and Norton equivalents are:




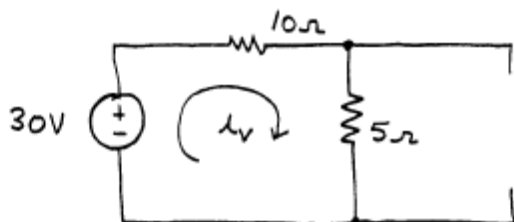P2.94\* First, we zero the current source and find the current due to the voltage source.



$$i_v = 30/15 = 2 \text{ A}$$

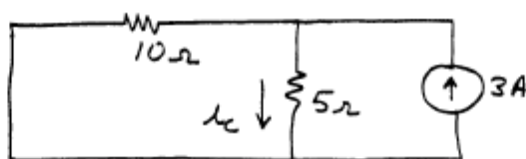Then, we zero the voltage source and use the current-division principle to find the current due to the current source.




$$i_c = 3 \frac{10}{5+10} = 2 \text{ A}$$


Finally, the total current is the sum of the contributions from each source.

$$i = i_v + i_c = 4 \text{ A}$$

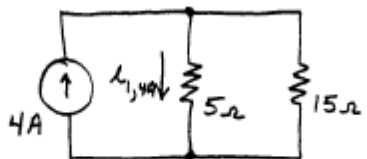P2.97 The circuits with only one source active at a time are:


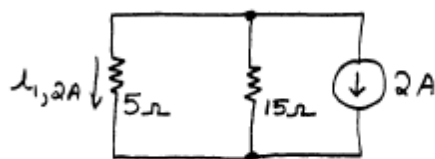
$$i_{1,4A} = 4 \times \frac{15}{15+5} = 3 \text{ A}$$



$$i_{1,2A} = -2 \times \frac{15}{15+5} = -1.5$$

Finally, we add the components to find the current with both sources active.

$$i = i_{1,4A} + i_{1,2A} = 1.5 \text{ A}$$