

# Amplifiers

- An *amplifier* creates a replica signal with a greater amplitude:
  - Higher voltage
  - or
  - Higher current
  - and/or
  - Higher power




# Amplifiers (cont.)

- Voltage amplifier:

$$v_o(t) = A_v v_i(t)$$


- The *voltage gain* is  $A_v$ .
- The voltage gain can be a positive number or a negative number.
  - *Inverting* amp has a negative gain
  - *Non-Inverting* amp as a positive gain

# Voltage Amplifier

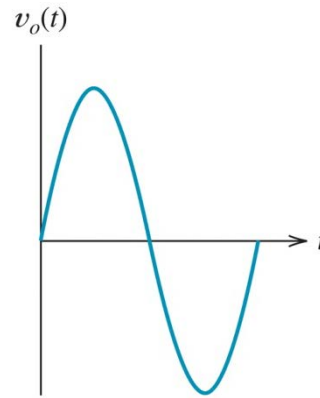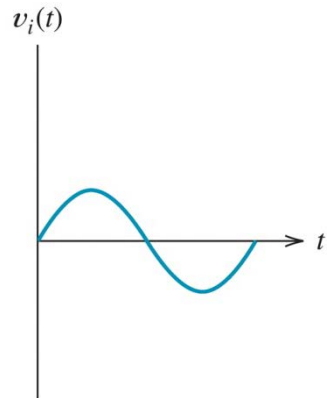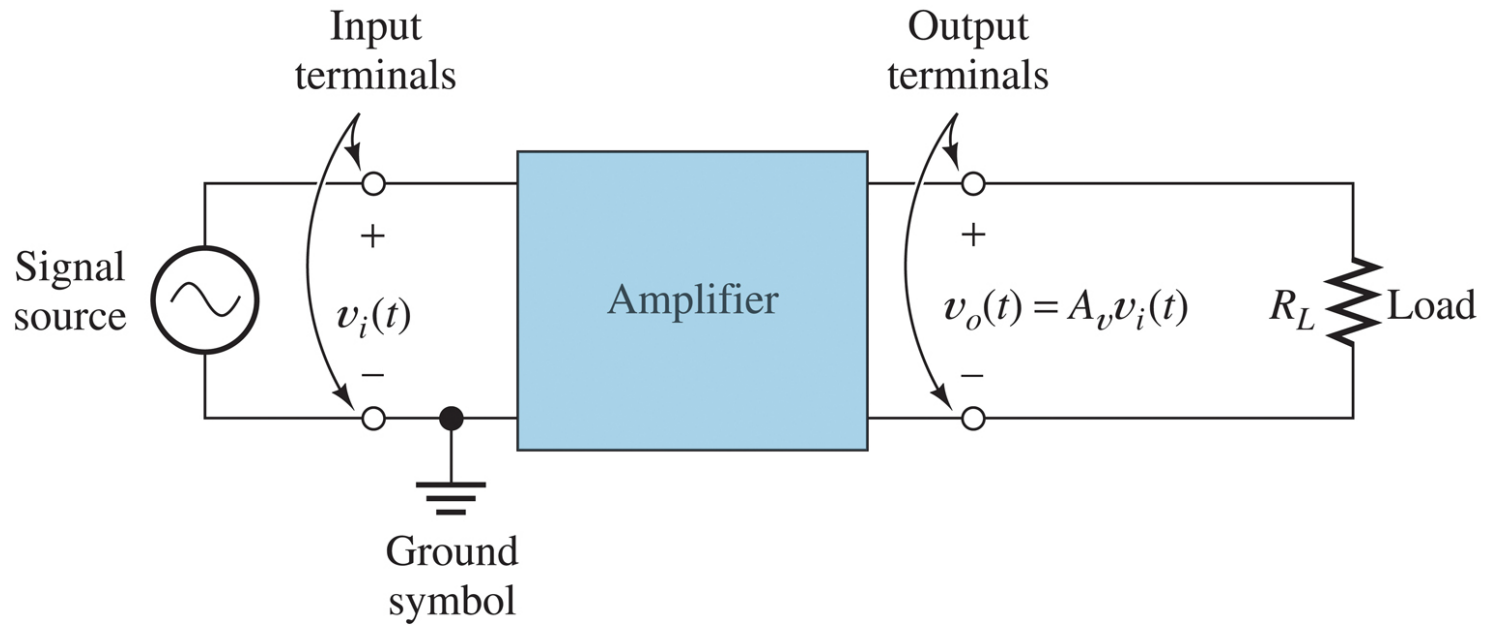

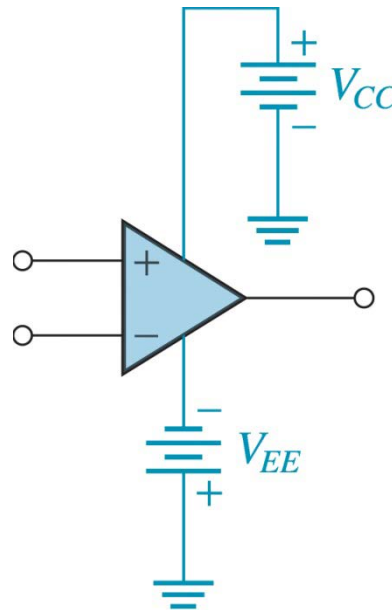
# Amplifiers (cont.)

- An amplifier requires a DC power source: the amp needs energy, because the power delivered to the load is greater than the power from the signal source itself.



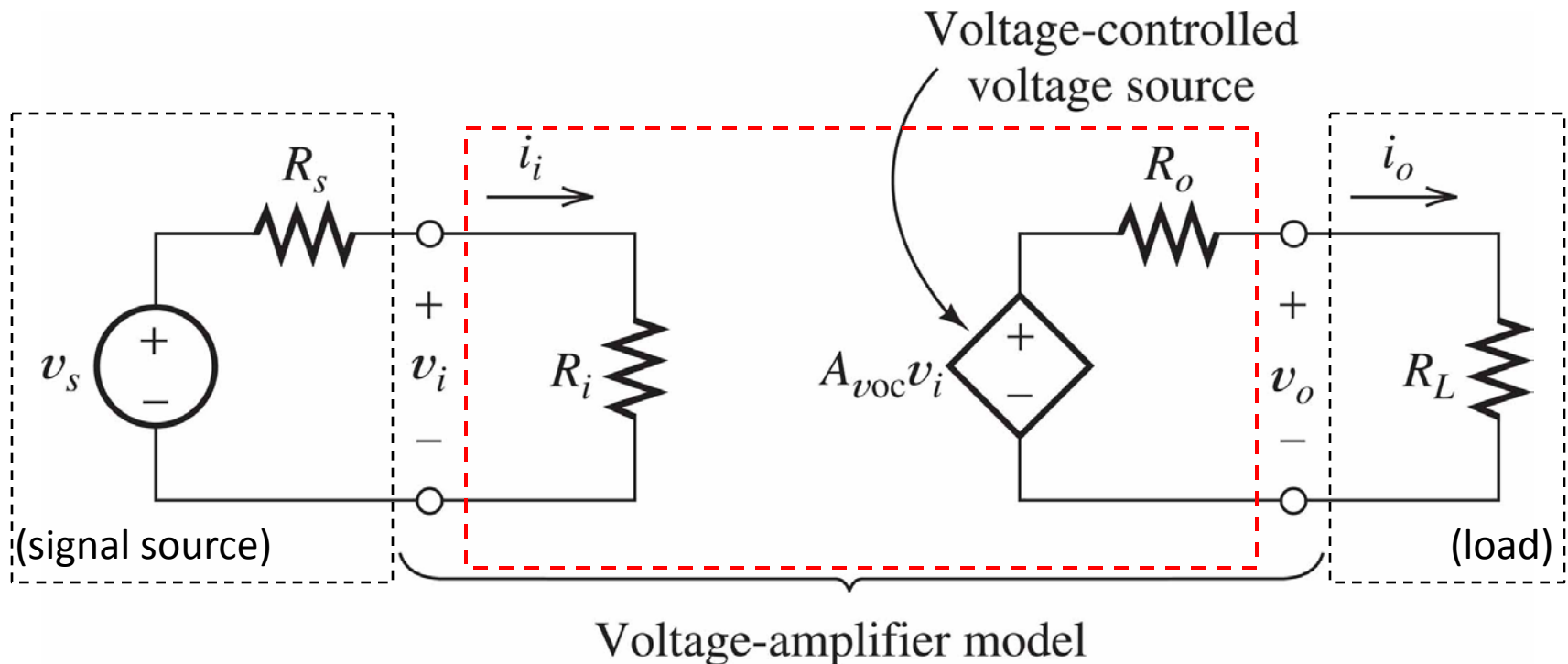
# Amplifiers (cont.)

- A realistic voltage amplifier model includes a *big* input resistance  $R_i$  (ideally infinite) and a *small* output resistance  $R_o$  (ideally zero).



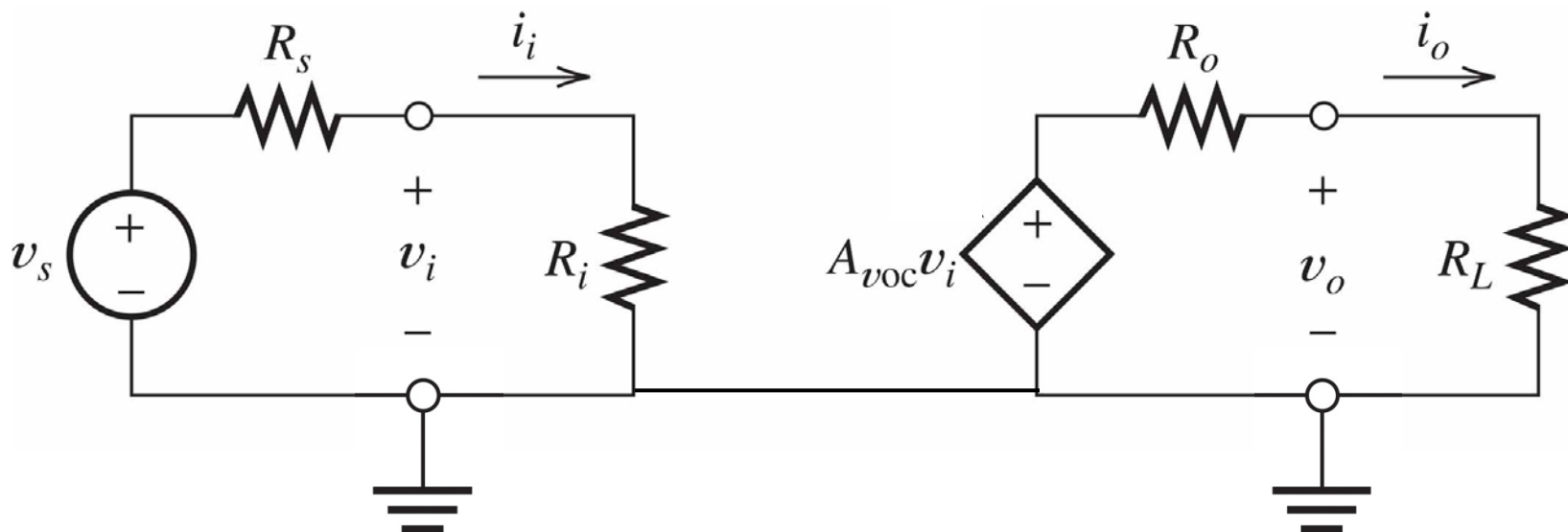
# Single-ended vs. differential

- Some amplifiers have a common ground between the input and the output. We call these “single-ended”


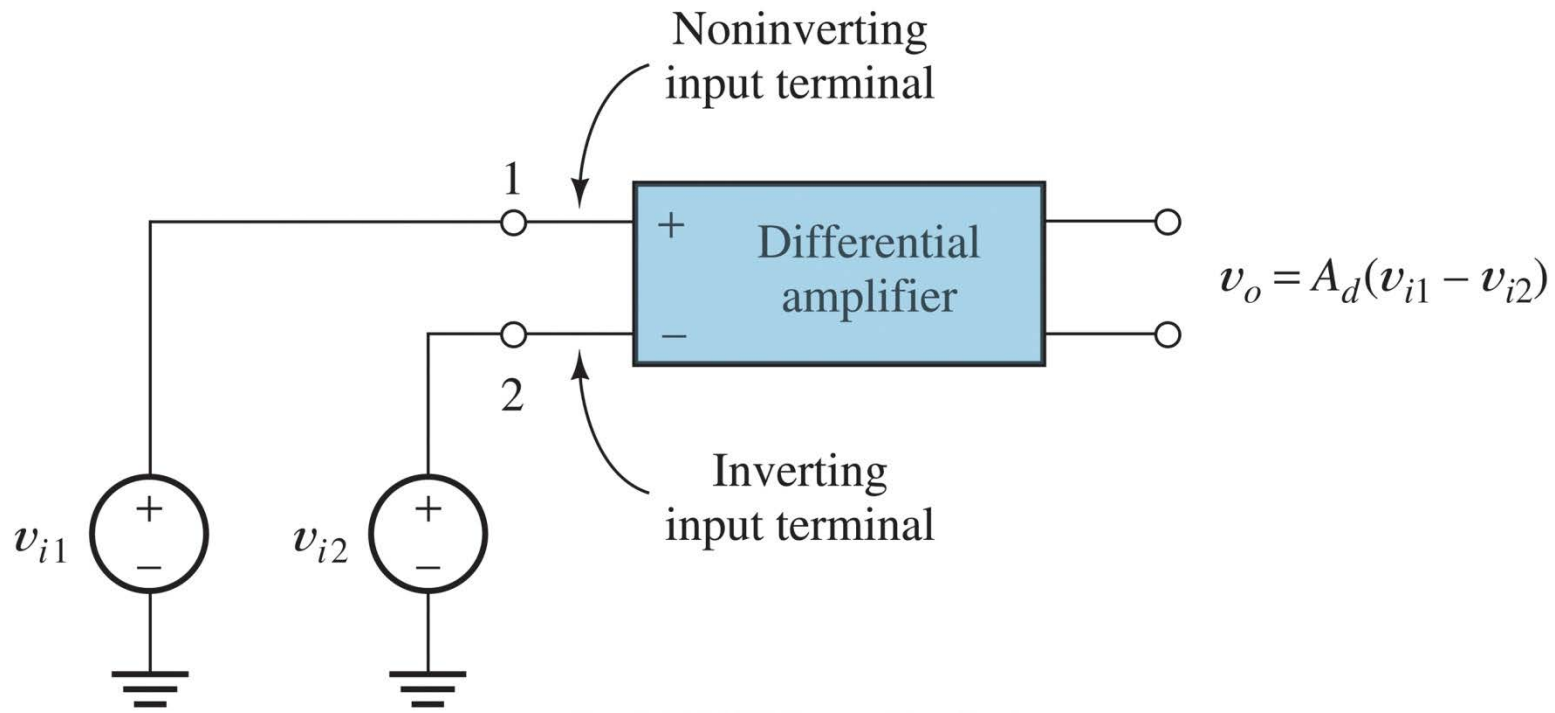
# Single-ended vs. differential (cont.)

- Some amplifiers amplify the *difference* between the voltages presented to its input pins, neither of which is grounded. These are called *differential* amplifiers.





# Node and ground notation

- So far in this course we have been writing circuit diagrams with explicit loops.
- For voltage amplifiers, a convenient shorthand notation is to depict a circuit in terms of its nodes and ground, rather than showing all the circuit loops.
- All of the circuit ground points are implicitly connected.



# Node and ground (cont.)

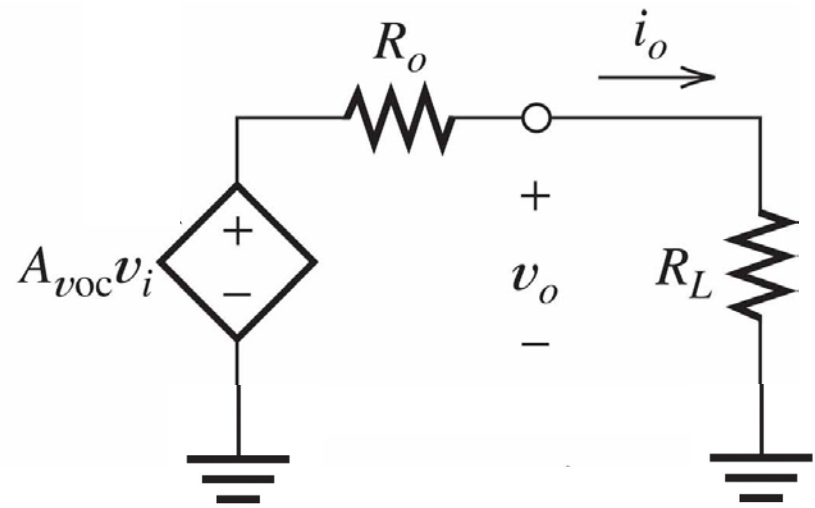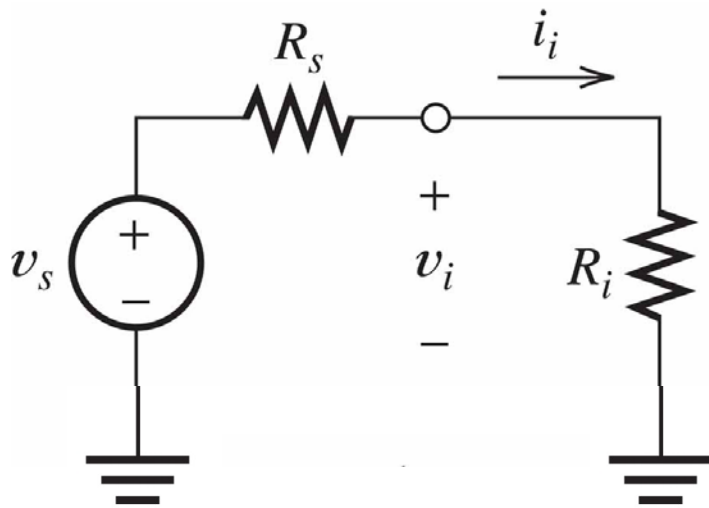


# The “Operational” Amplifier

- The “op amp” is a differential input, single-ended output voltage amplifier.
- The op amp has:
  - very high input resistance
  - very low output resistance
  - very high voltage gain
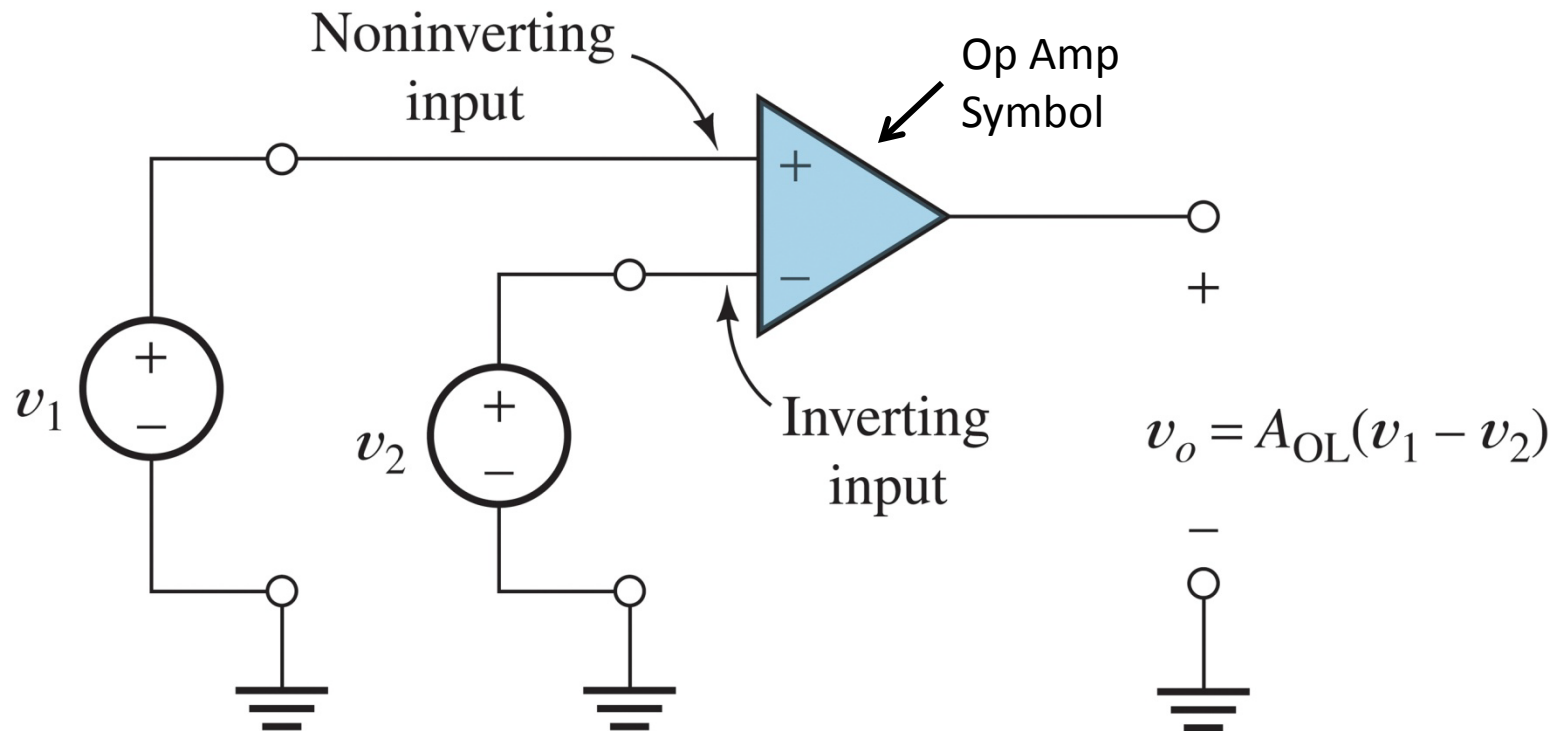
# The Ideal Op Amp

- A “perfect” op amp would have infinite input resistance, zero output resistance, and voltage gain  $A_{OL}$  (open loop) approaching infinity.



# Negative Feedback

- NOTE that if the op amp's output voltage is a finite value, the differential input voltage will be tiny. In other words, since:

$$A_v = V_o / V_{in}$$

If  $A_v \rightarrow \text{infinity}$  and  $V_o$  is finite,


$V_{in}$  must be REALLY small ( $V_{in} \rightarrow 0$ )

- Most op amp circuits have deliberate feedback from the output back to the *inverting* input. This is called *negative feedback*.


# Negative Feedback (cont.)

- “Ideal” op amp assumptions if negative feedback is present:
  1. Differential input voltage is zero, so + input and – input are the same voltage
  2. Input current is zero
  3. Then analyze circuit using regular techniques to find voltage gain  $v_o / v_i$

# Ideal Op Amp Example

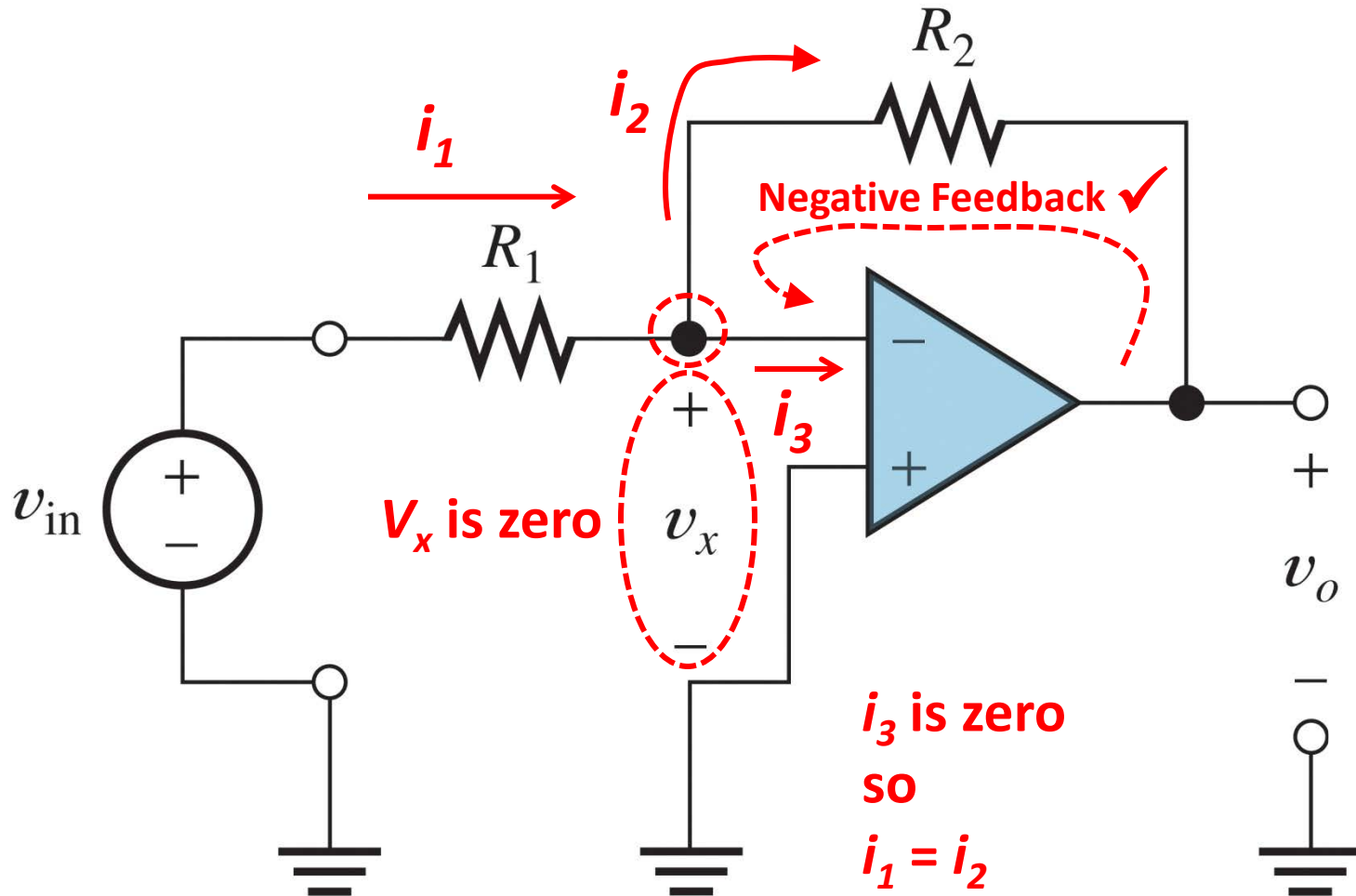

# Ideal op amp (cont.)

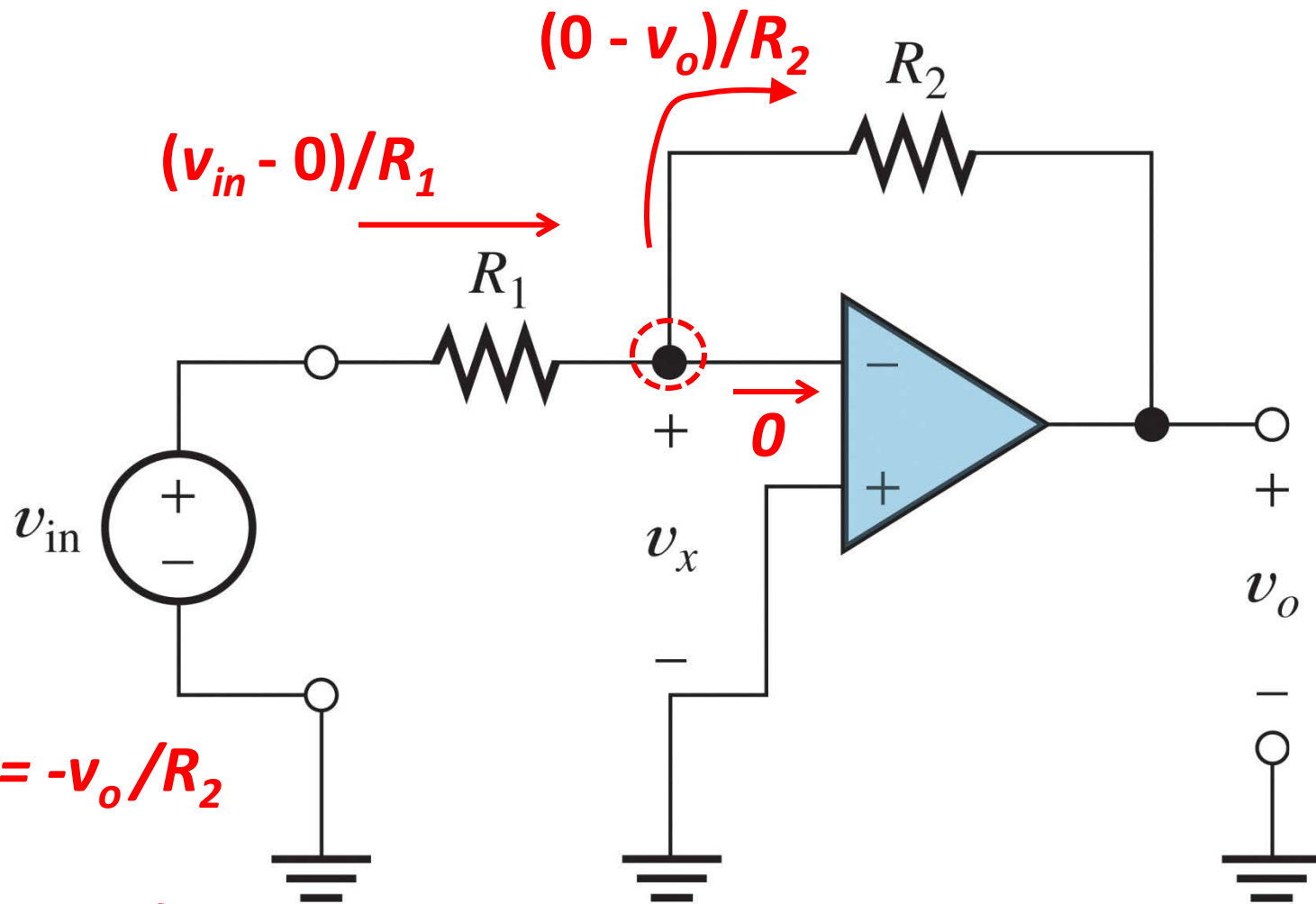

$$V_{in}/R_1 = -v_o/R_2$$

$$V_o/v_{in} = -R_2/R_1$$

# Ideal Op Amp Summary

- High open-loop gain and negative feedback forces differential input voltage to be zero
- High input resistance forces input current to be zero
- Use these assumptions to analyze the closed-loop gain

